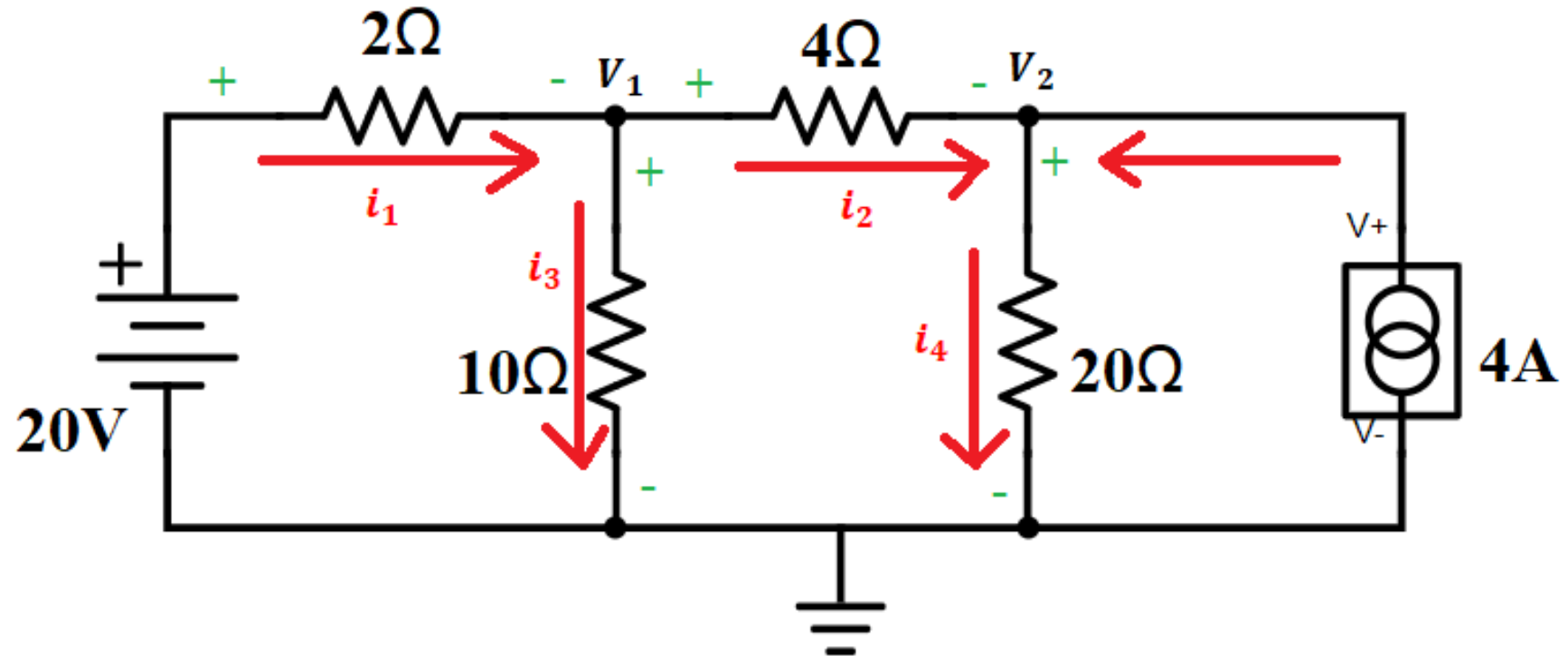


# TOPIC #3 CKT Analysis


---


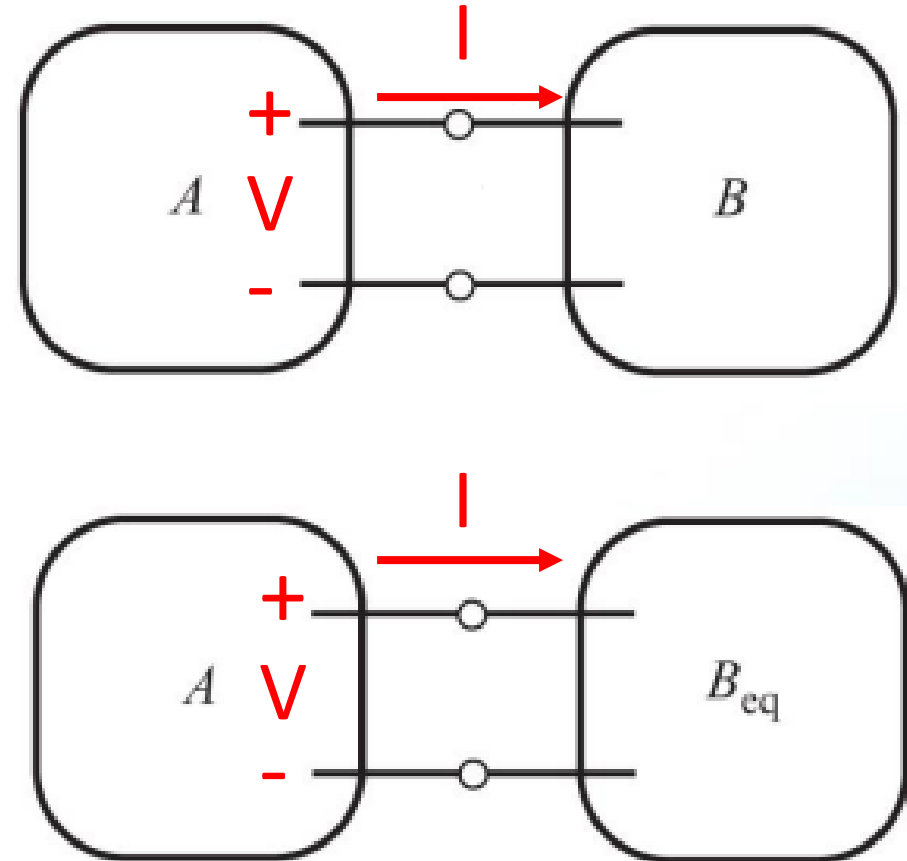
# Circuit model



- Circuit model

- The  $V/I$  output behavior of  $A$  is independent of the load  $B$ .
- Usually, we have Thevenin and Norton equivalence circuit
- The main purpose of the circuit model is to focus on the circuit behavior but not how to construct the circuit


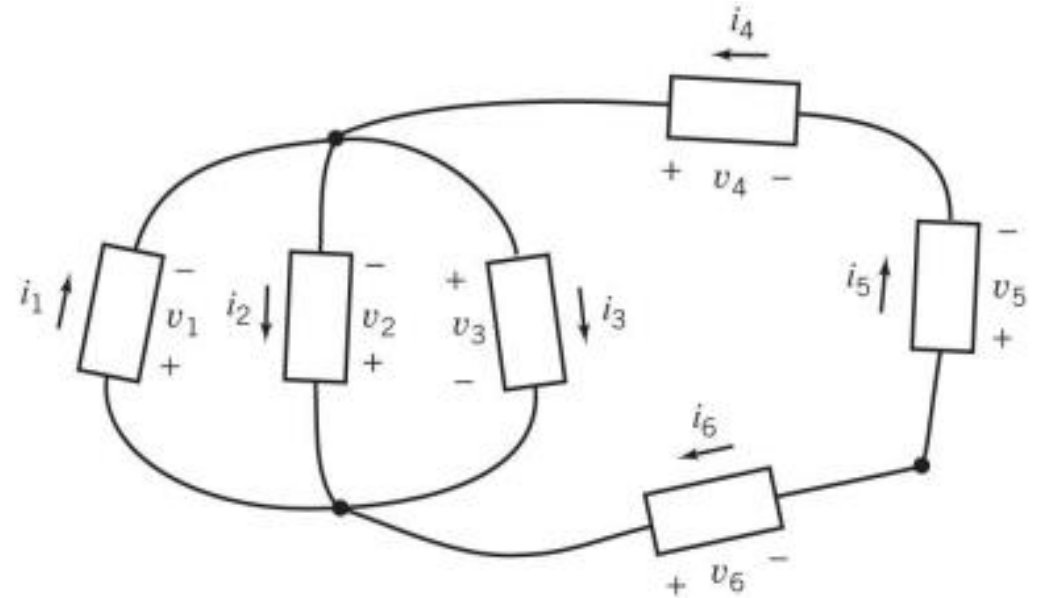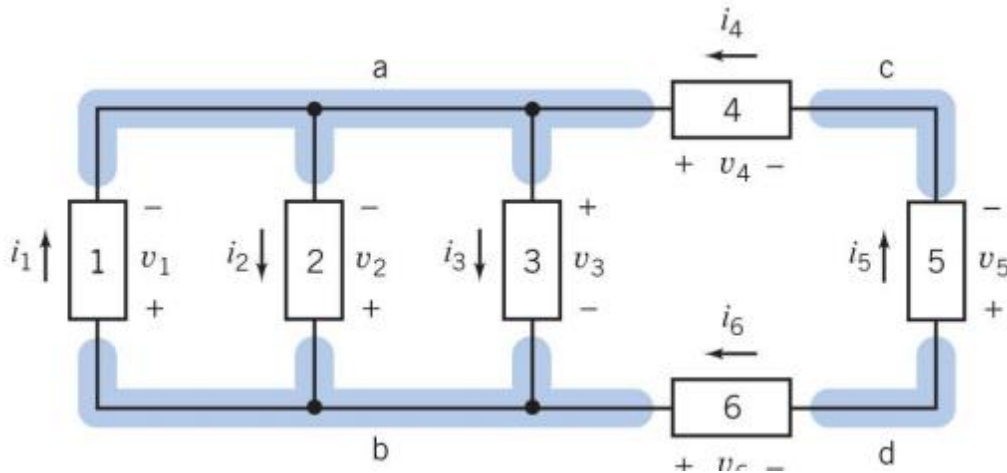
# Kirchhoff's Laws(1/5)

- A node is a point where two or more circuit elements join
  - If only two elements connect to form a node, they are in series
  - Elements in series share the same current
- Closed path: a loop starting and ending at the same node and pass intermediate nodes only once



# Kirchhoff's Laws(2/5)

---

- Kirchhoff's current law (KCL)
  - For any node, the algebraic sum of all the currents equals to zero

$$\sum_n i_n = 0$$

Charge conservation

Kirchhoff's voltage law (KVL)


- For any closed path, the algebraic sum of all the voltages equals to zero

$$\sum_n V_n = 0$$

Energy conservation

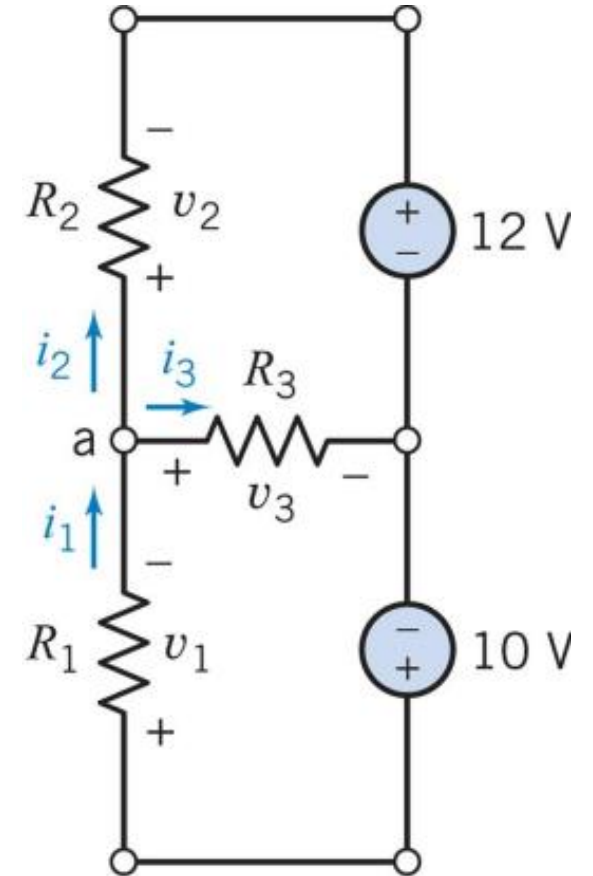
# Kirchhoff's Laws(3/5)

- Find each current and each voltage when  $R_1 = 8\ \Omega$ ,  $v_2 = -10\text{ V}$ ,  $i_3 = 2\text{ A}$ , and  $R_3 = 1\ \Omega$ . Also, determine the resistance  $R_2$ .




# Kirchhoff's Laws(4/5)

- Determine the value of the current

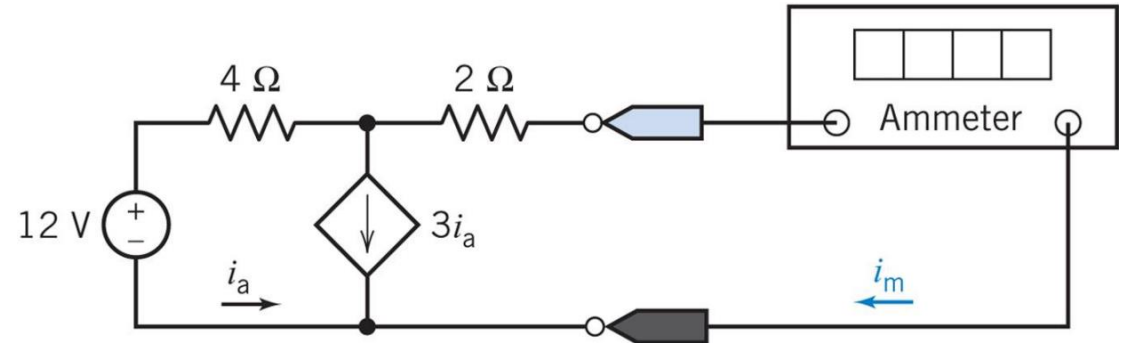

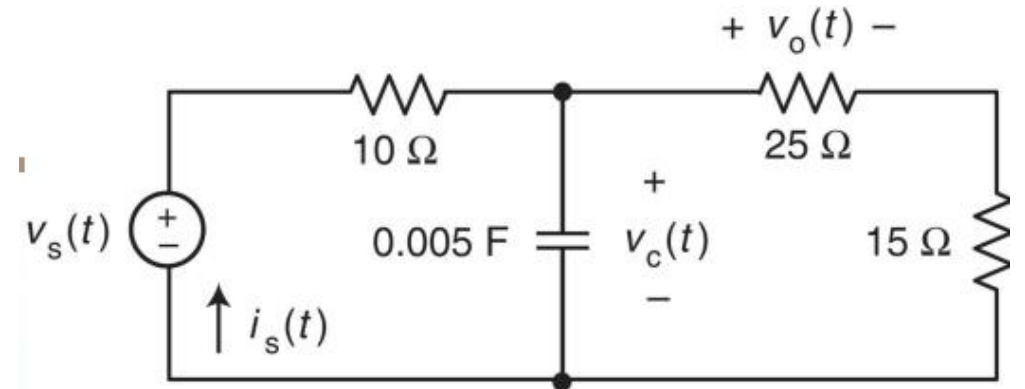
# Kirchhoff's Laws(5/5)

- Find  $V_o(t)$  when
  - $V_s(t) = 50 \text{ V}$ ;  $V_c(t) = 40 - 40e^{-25t} \text{ V}$


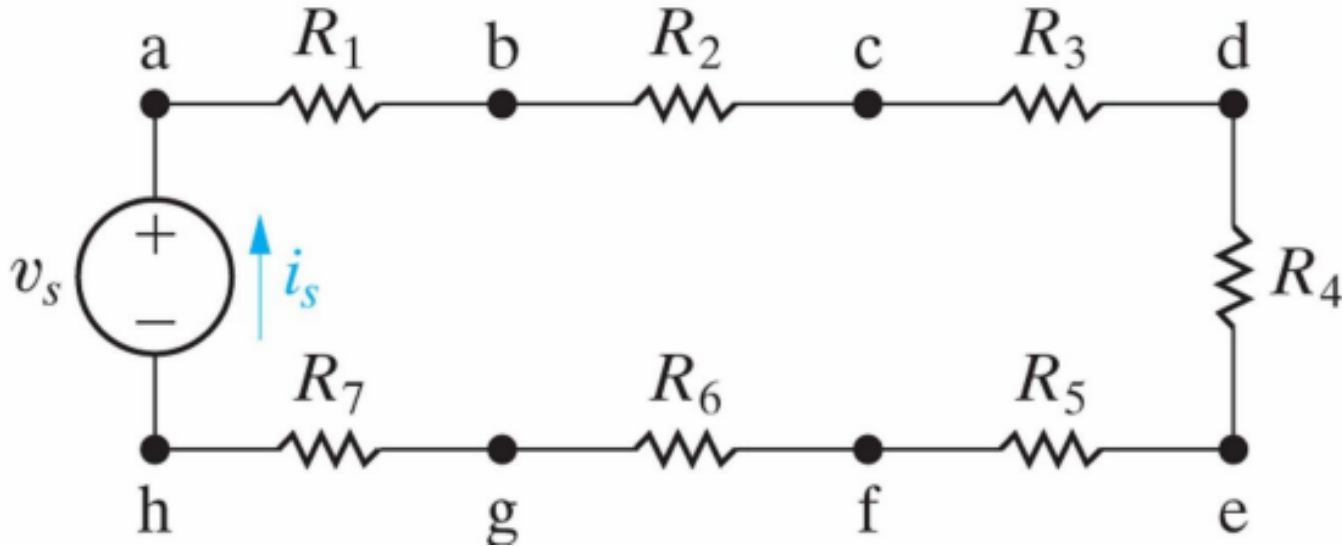
# Voltage division (1/2)

- KCL: all resistors have the same current
- Used to find the voltage drop across a single resistance from a collection of series-connected resistance.




$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_k} \cdot v_s$$



# Voltage division(2/2)


- Find  $V_2$

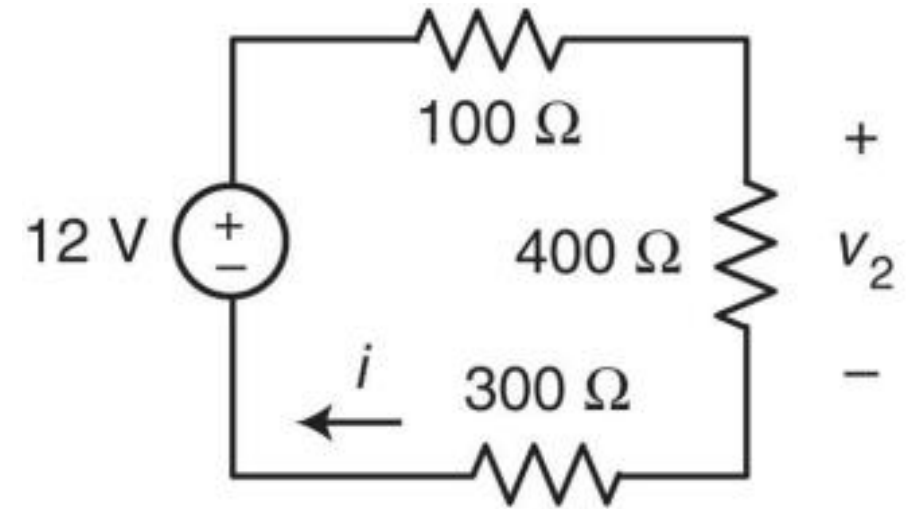
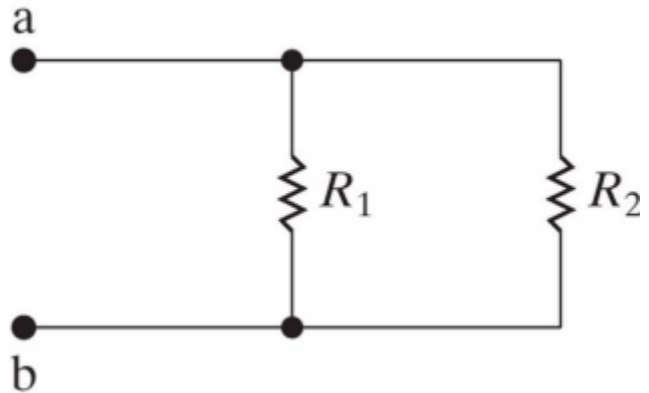
# Resistors in Parallel(1/2)

---

- Equivalent resistance  $R_{eq}$  is always smaller than the minimum resistance in parallel connection
- And the **smallest resistance** dominates the equivalent value
  - Why? Because more current is needed to satisfy KVL
- When we only have two resistors in parallel
  - Current inversely proportional




$$R_{eq} = \frac{(R_1 R_2)}{(R_1 + R_2)}$$

$$i_2 = \frac{R_1}{(R_1 + R_2)} i_s$$

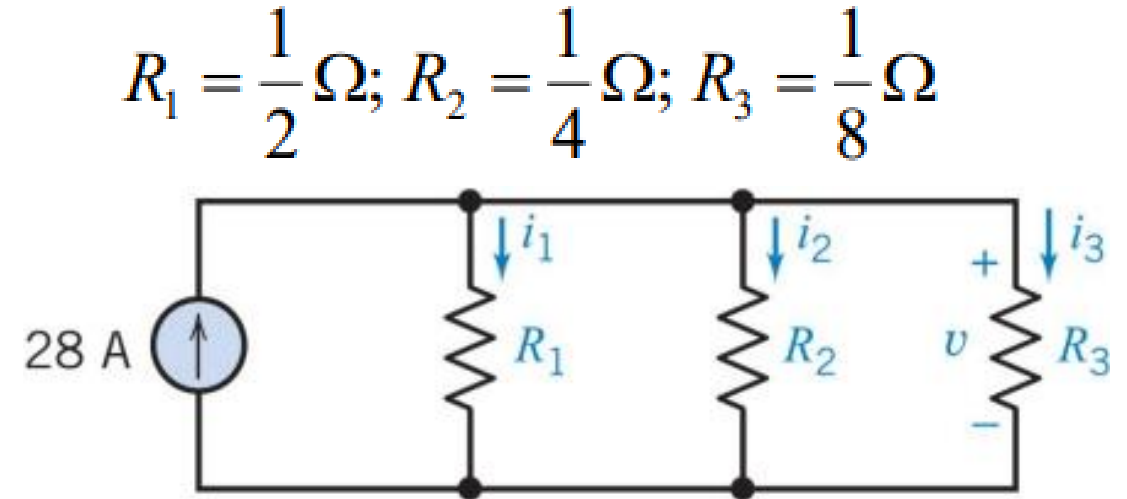
# Resistors in Parallel(2/2)

- Find
  - (a) the current in each branch,
  - (b) the equivalent circuit, and
  - (c) the voltage  $v$ .



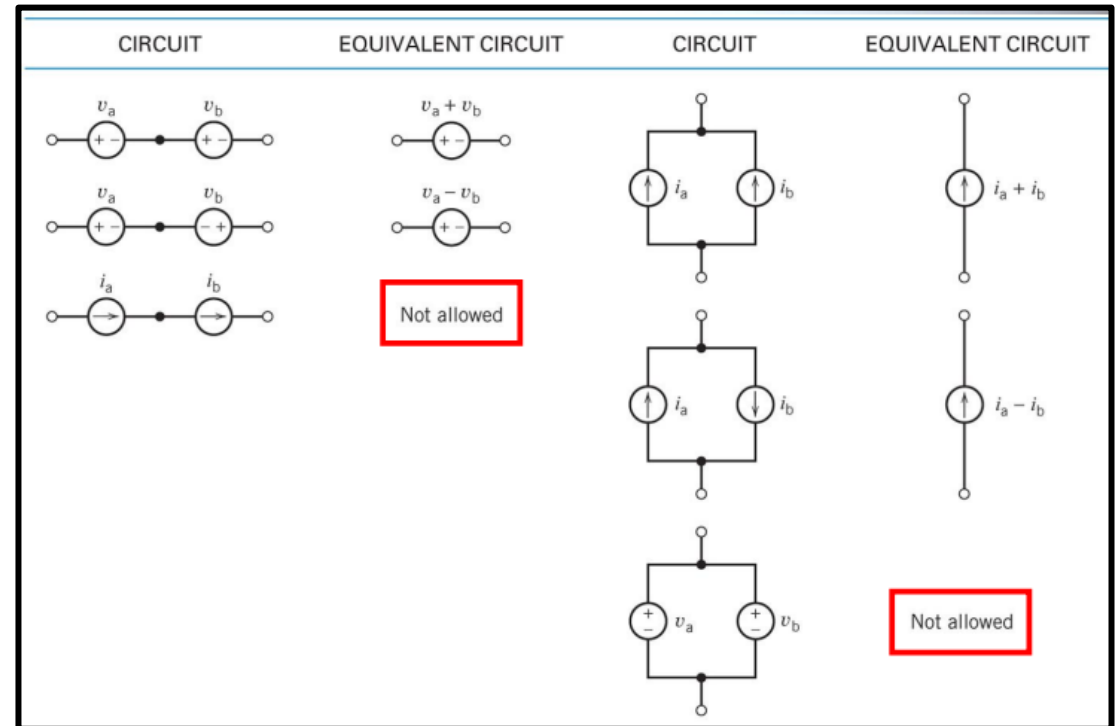
# Circuit analysis(1/5)

- Voltage sources connected in series  $\leftrightarrow$  a single voltage source
  - The voltage of the equivalent voltage source is equal to the algebraic sum of voltages of the series voltage sources
- Same concept for current sources



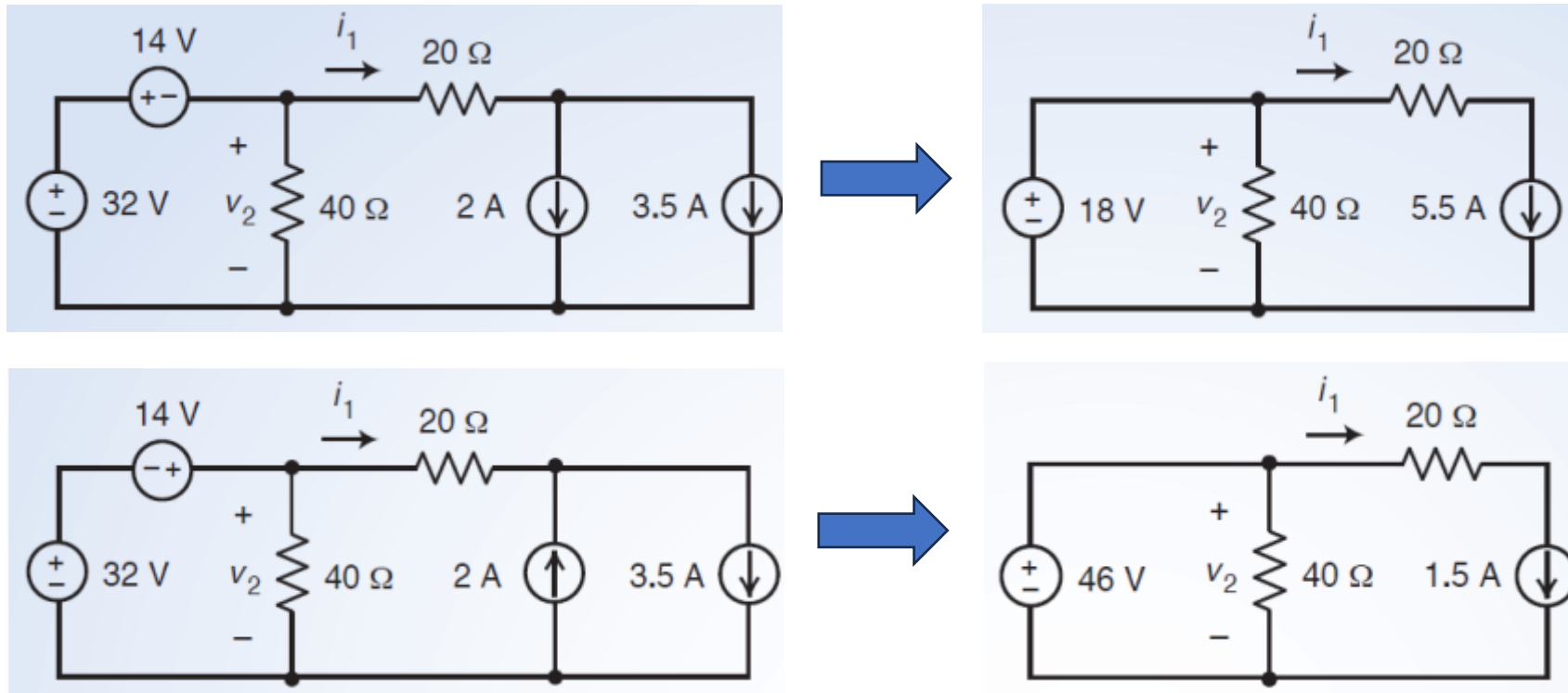
# Circuit analysis(2/5)

- In each circuit, replace the series voltage sources with an equivalent voltage source and the parallel current sources with an equivalent current source



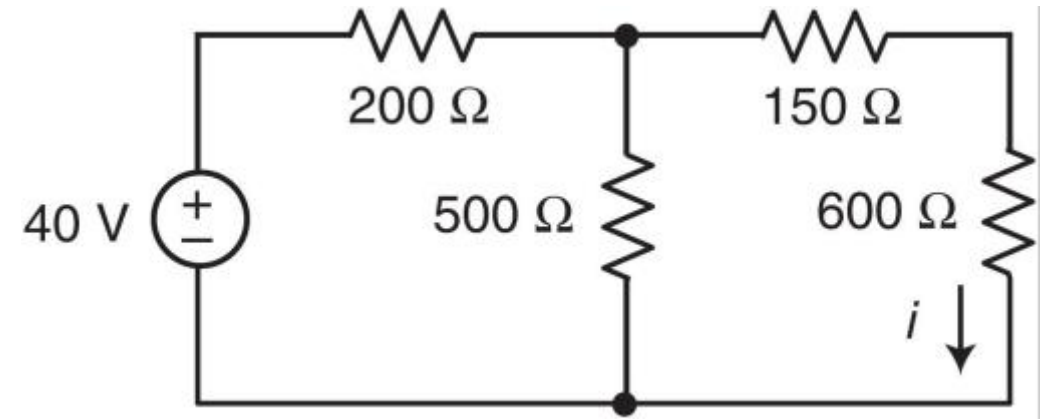
# Circuit analysis(3/5)

- Determine the value of the current  $i$




# Circuit analysis(4/5)

- Determine the resistance measured

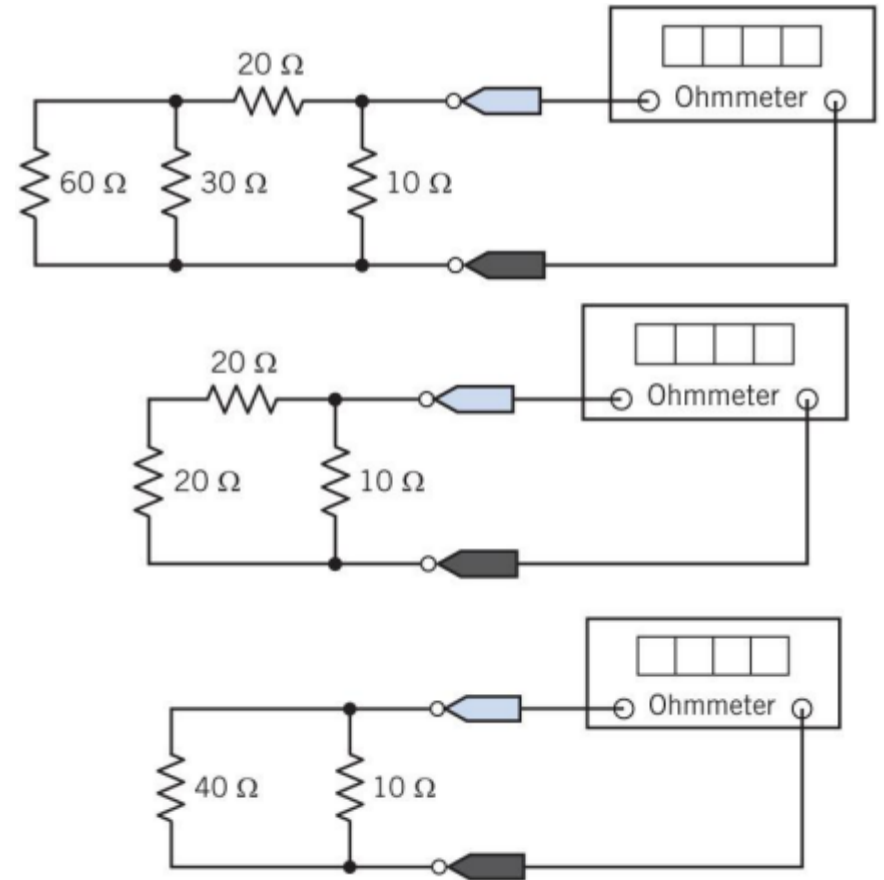
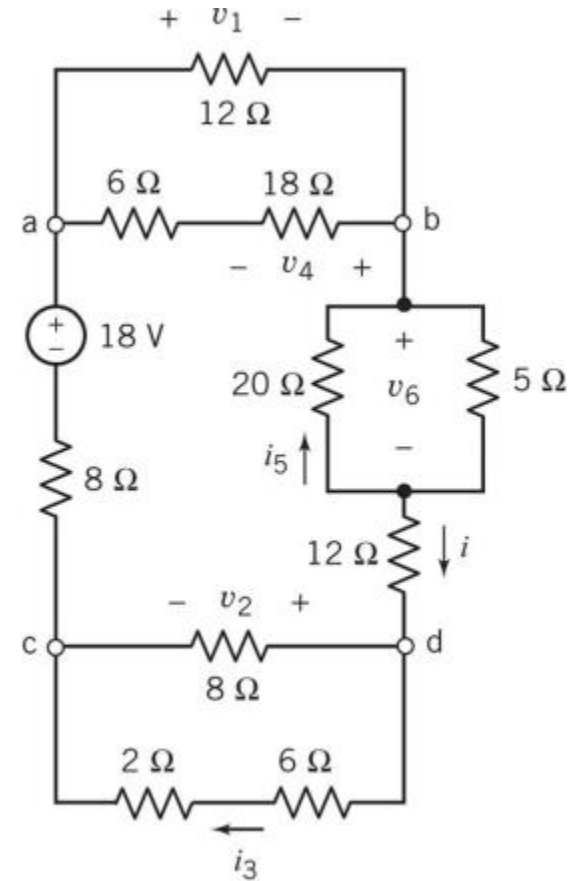
# Circuit analysis(5/5)

- Determine the values of  $i_3$ ,  $v_4$ ,  $i_5$ , and  $v_6$  (pay attention to sign)





# Defining various terms


---

- Number of essential branch ( $b_e$ ) identifies the total unknowns

Name	Definition
node	A point where two or more circuit elements join
essential node	A node where three or more circuit elements join
path	A trace of adjoining basic elements with no elements included more than once
branch	A path that connects two nodes
essential branch	A path which connects two essential nodes without passing through an essential node
loop	A path whose last node is the same as the starting node
mesh	A loop that does not enclose any other loops
planar circuit	A circuit that can be drawn on a plane with no crossing branches



# Node, branch, mesh and loop

- 6 unknown currents

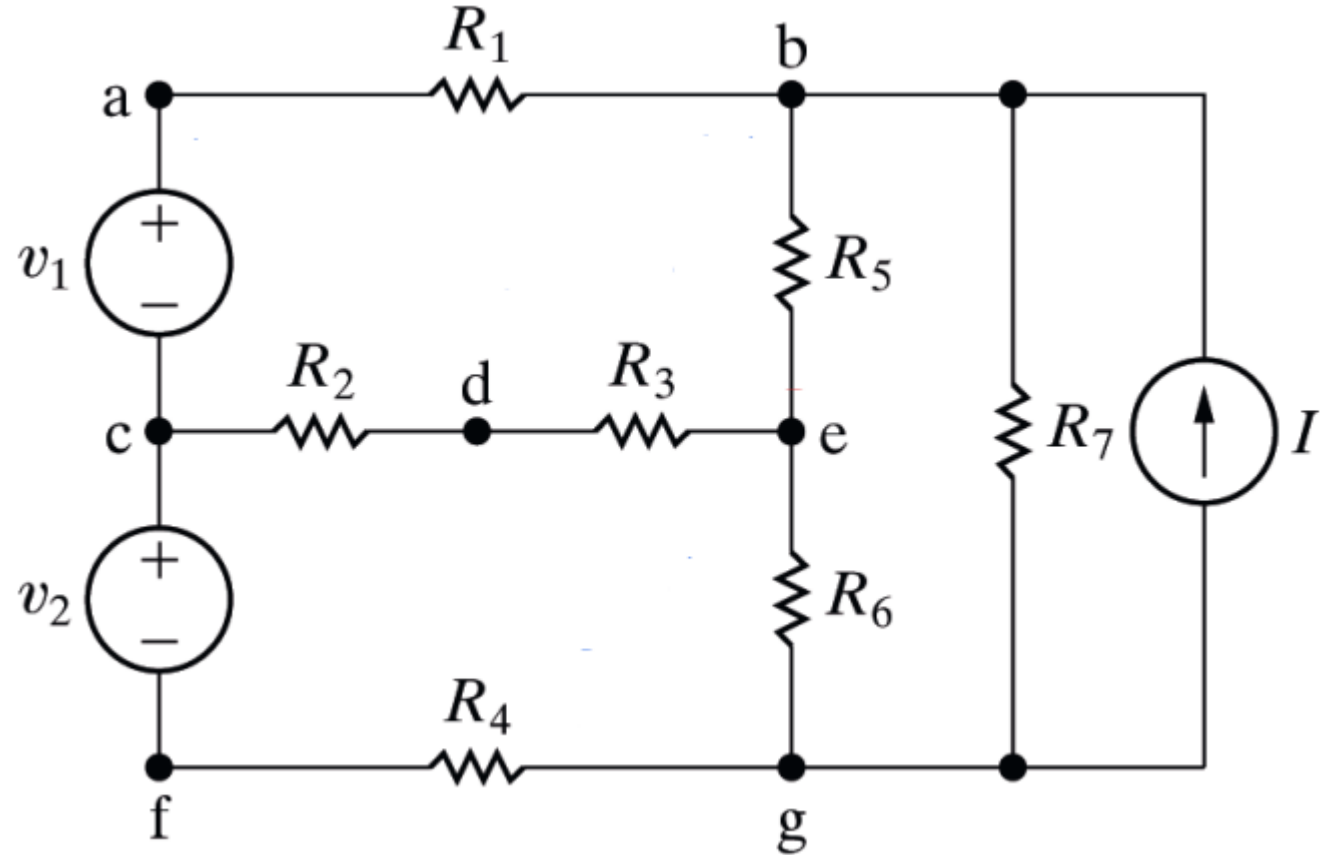

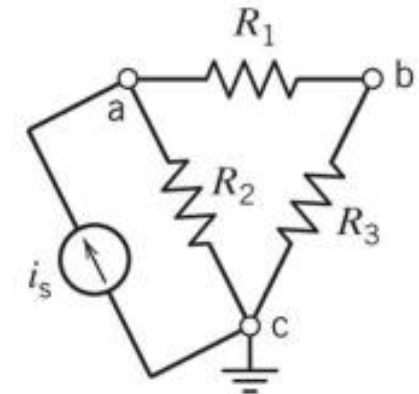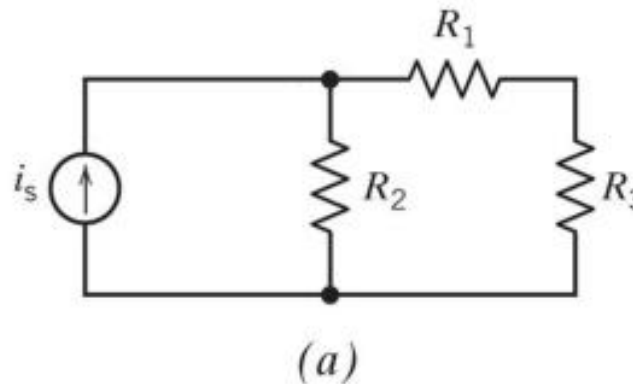
# Node-Voltage Method(1/6)

- Meant to simplify our circuit analysis
- A reference node is chosen from among the essential nodes
- Steps:
  1. Identify essential node
  2. Choose an essential node as ground
  3. Using KCL to find the parameters of others node
  4. Super node



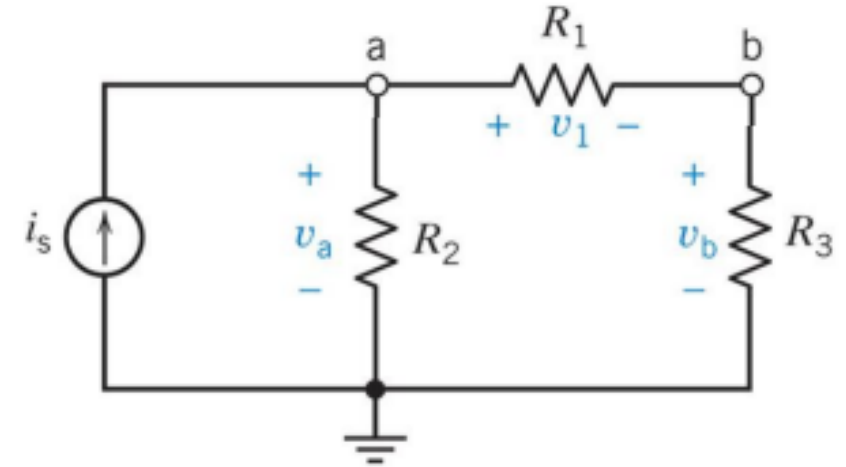
# Node-Voltage Method (2/6)

- Writing out the equation sets
  - Do you need to write down KCL for node b?
- If  $R_1 = 1\Omega$ ;  $R_2 = R_3 = 0.5\Omega$ , and  $i_s = 4\text{ A}$



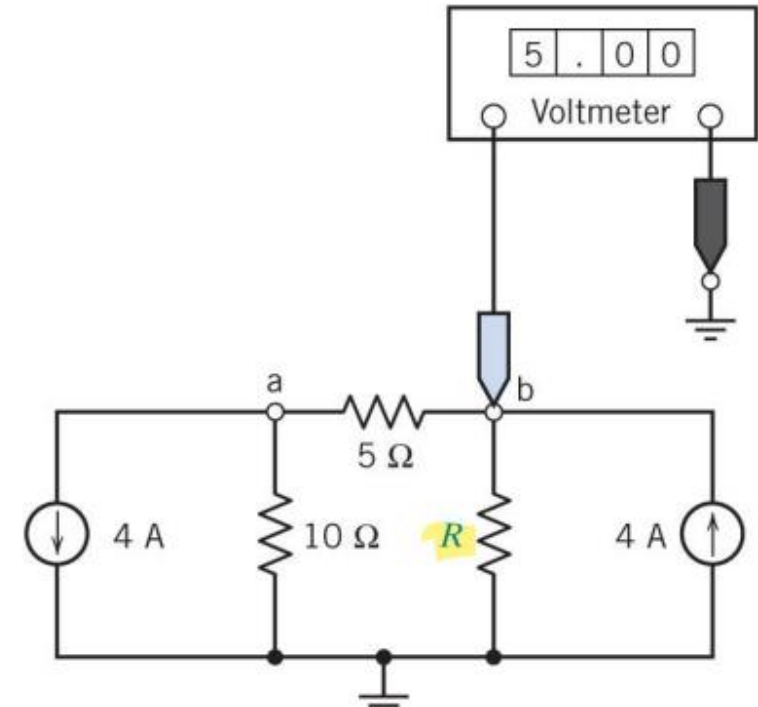
# Node-Voltage Method (3/6)

- Writing out the equation sets
  - Do you need to write down KCL for node b?
- If  $R_1 = 1\Omega$ ;  $R_2 = R_3 = 0.5\Omega$ , and  $i_s = 4\text{ A}$



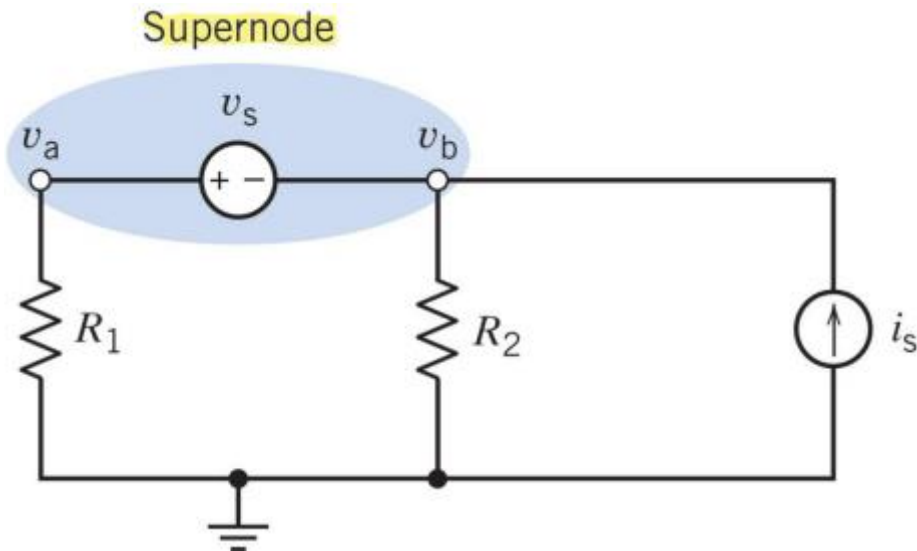
# Node-Voltage Method (4/6)

- Introducing **supernode**
- Two nodes connected by an independent or a dependent voltage source


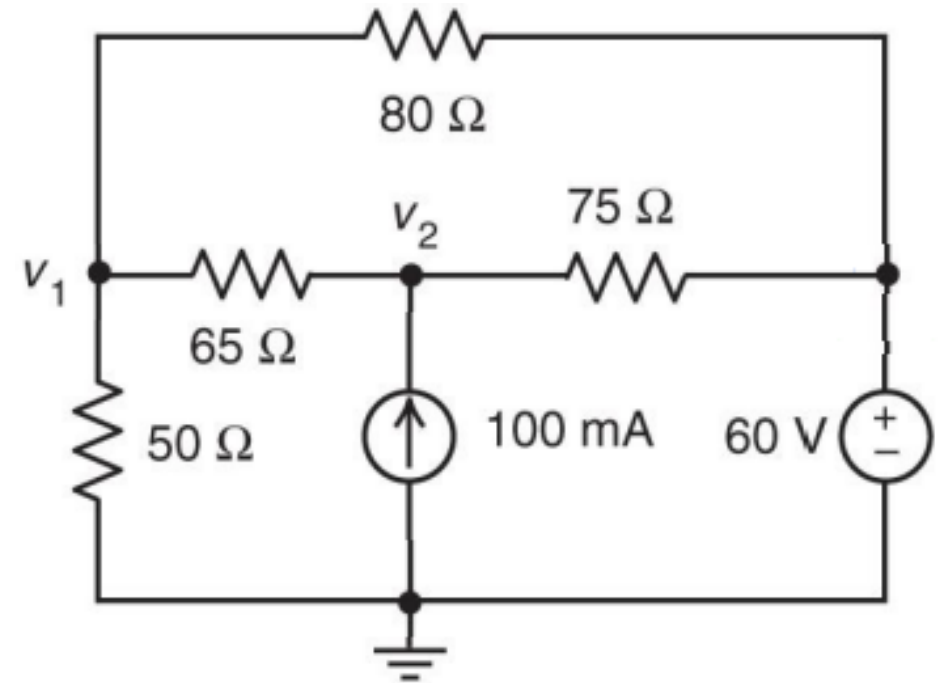
# Node-Voltage Method (5/6)


- Determine the node voltages  $V_1$  and  $V_2$


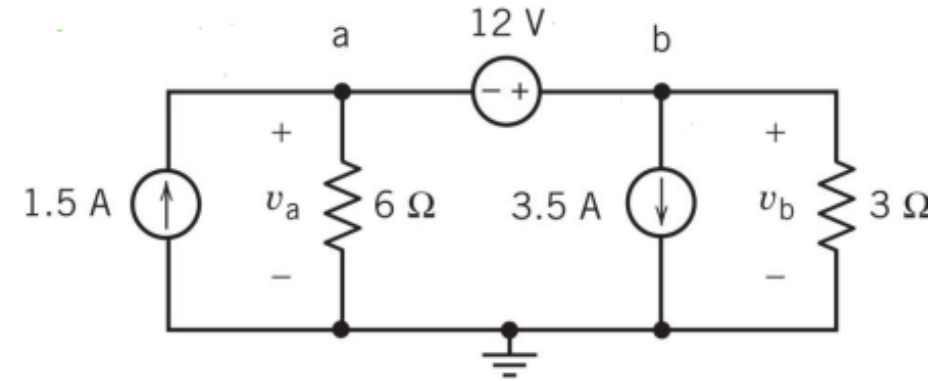
# Node-Voltage Method (6/6)

---



- Determine the values of the node voltages  $V_a$  and  $V_b$





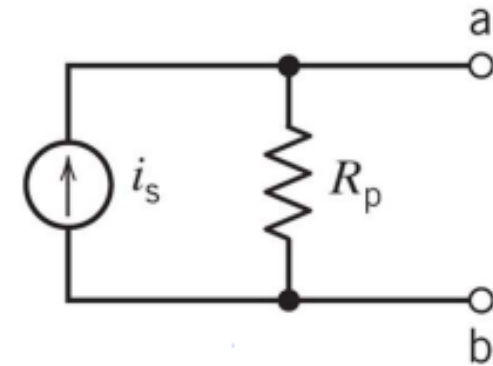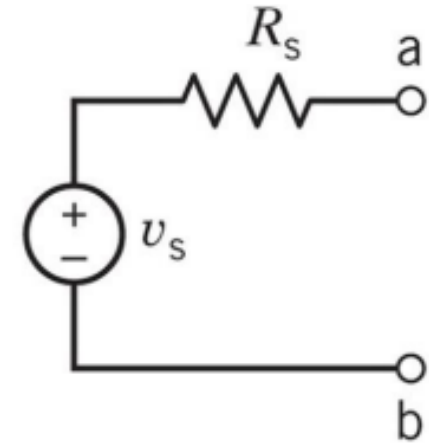
# Source transformations(1/3)

- In reality, we have nonideal sources
- What is an ideal source?
  - Voltage source
    - 100% of the voltage can be applied to the load
  - Current source
    - 100% of the current can be applied to the load
- Real sources: we have loss!
  - Voltage source
    - Need to add series resistance  $R_s$
  - Current source
    - Need to add parallel resistance  $R_p$



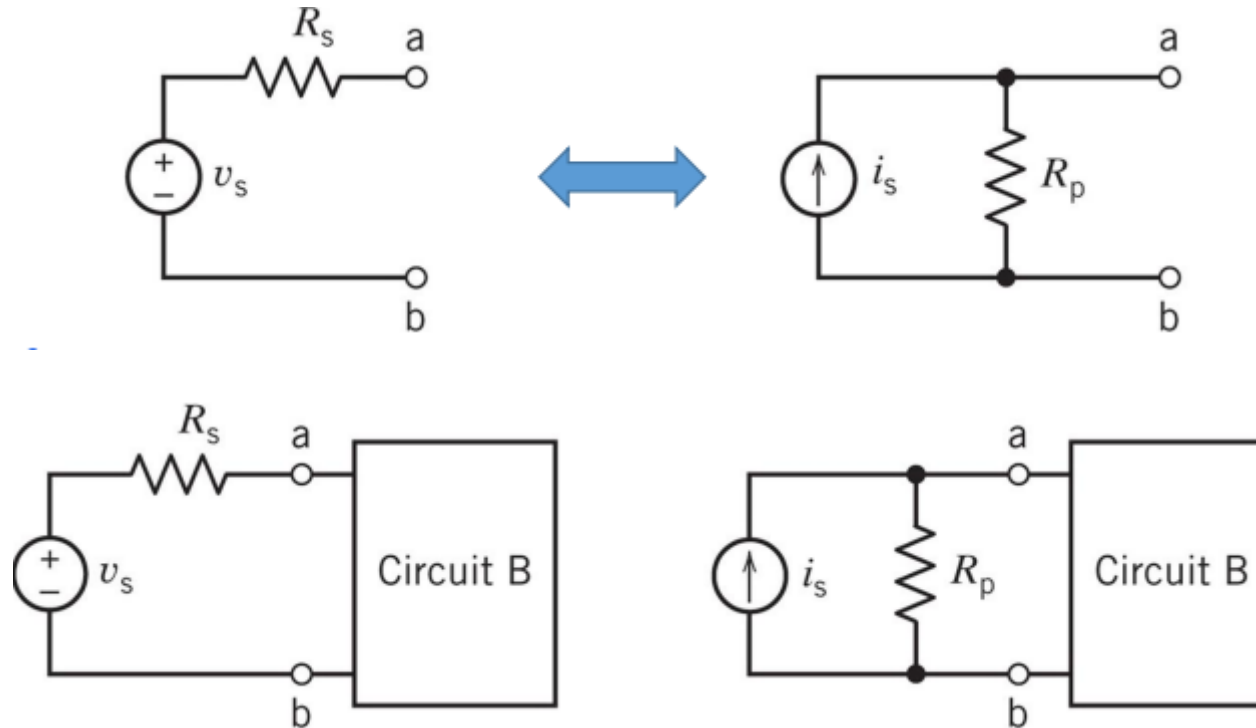
# Source transformations (2/3)

- Allows real voltage/current sources to be interchanged
- How to determine the parameters?
  - Let's connect a load between a and b




# Source transformations (3/3)

Thévenin equivalent ckt

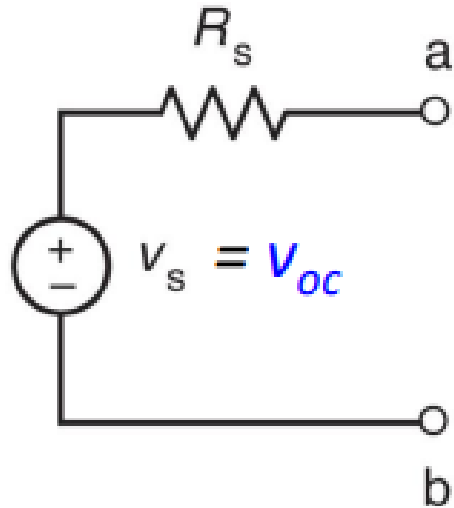

$$v_s = R_p i_p \text{ and } R_s = R_p$$





Norton equivalent ckt

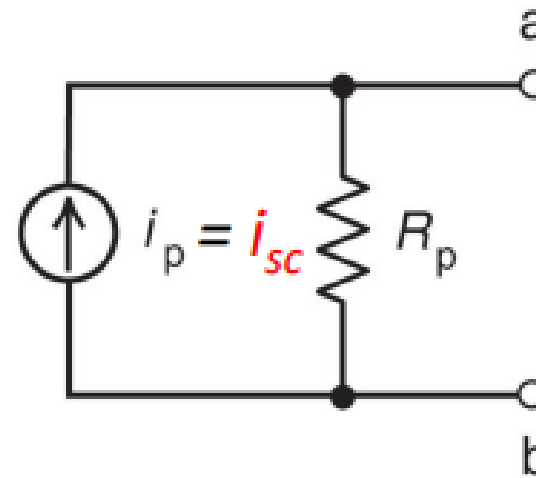

$$i_p = \frac{v_s}{R_s} \text{ and } R_p = R_s$$

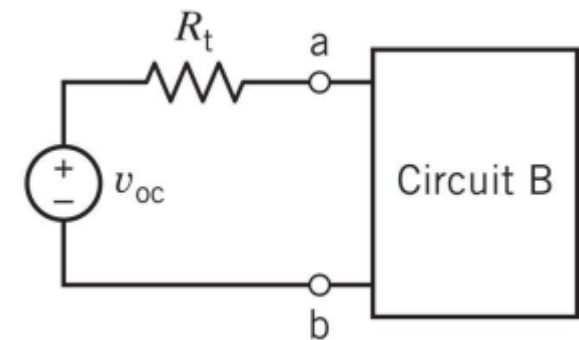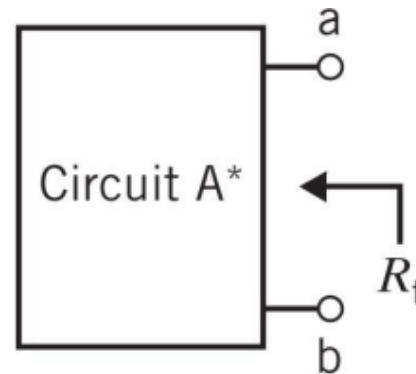
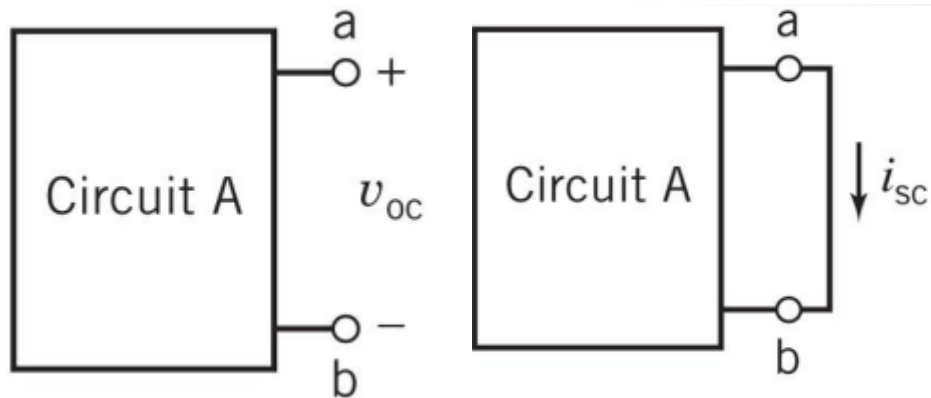
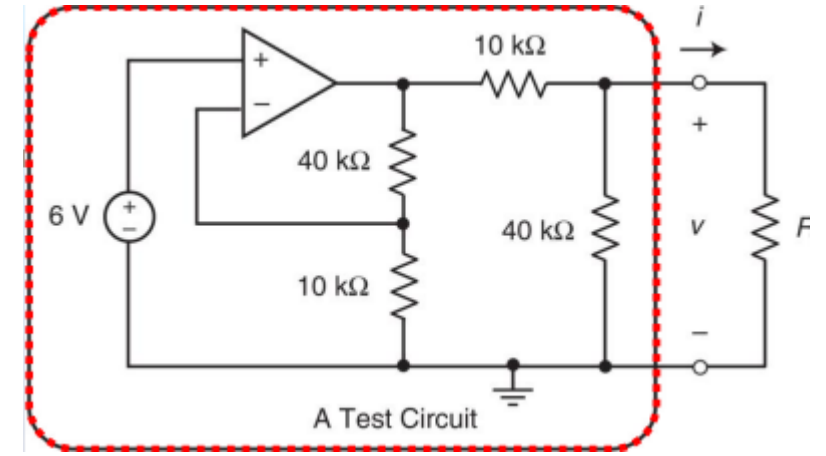
# Thévenin equivalent ckt(1)

- Thévenin equivalent ckt
  - Open-circuit voltage:  $V_{oc}$  or  $V_{Th}$
  - Short-circuit current:  $i_{sc}$
  - Thévenin resistance:  $R_t$  or  $R_{Th}$



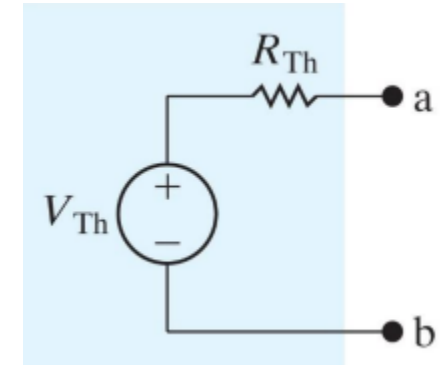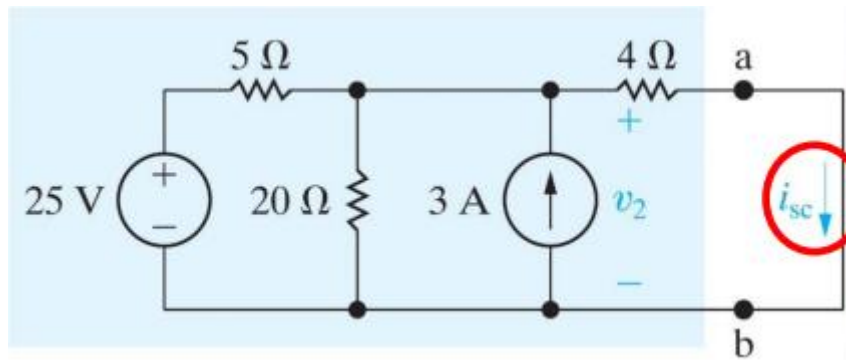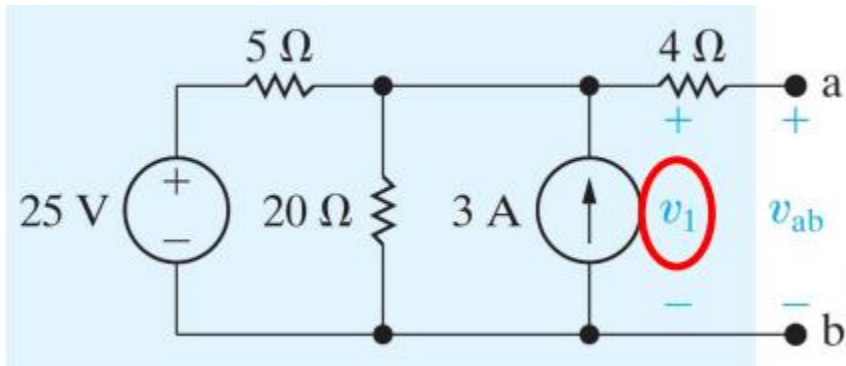
# Thévenin equivalent ckt(2)

- Method 1: the obedient way
  - Find open circuit voltage  $\rightarrow V_{th}$
  - Find short circuit current  $\rightarrow i_{sc}$


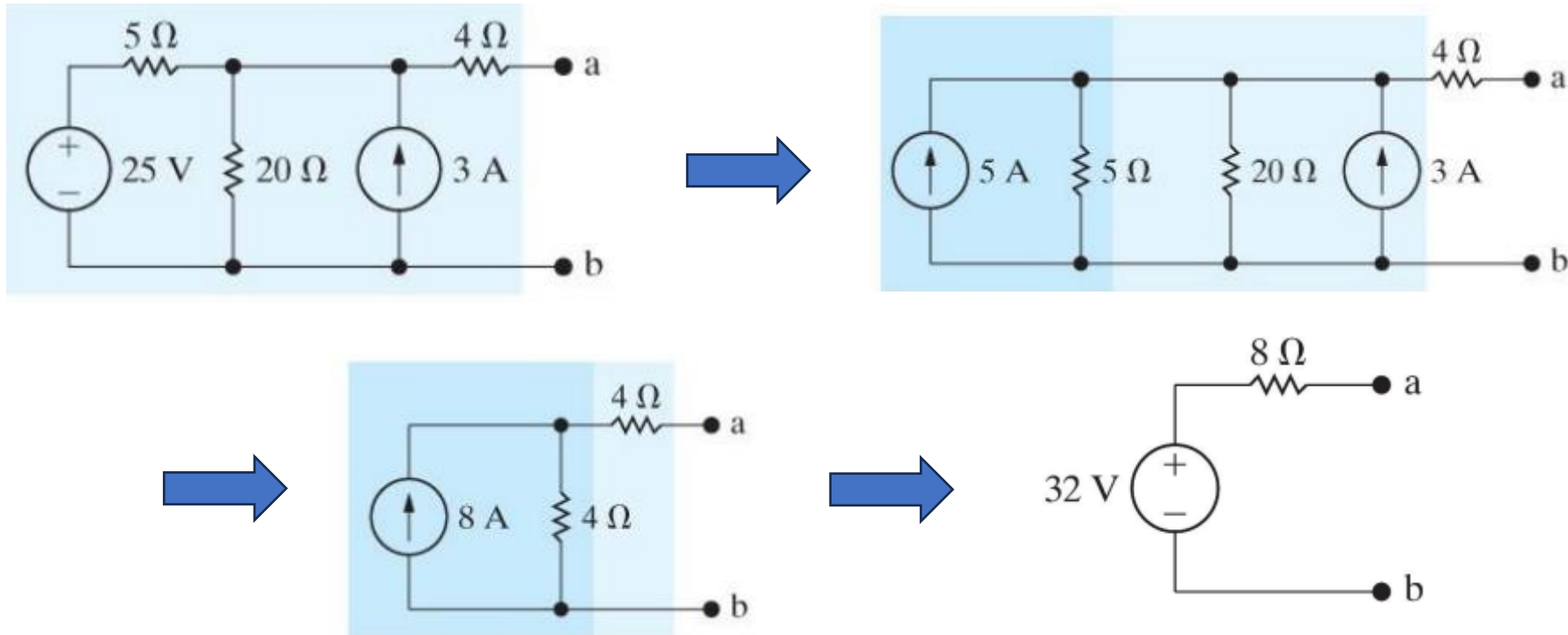
# Thévenin equivalent ckt(3)




- Method 2:
  - Use series source transformation when circuit contains ONLY independent sources


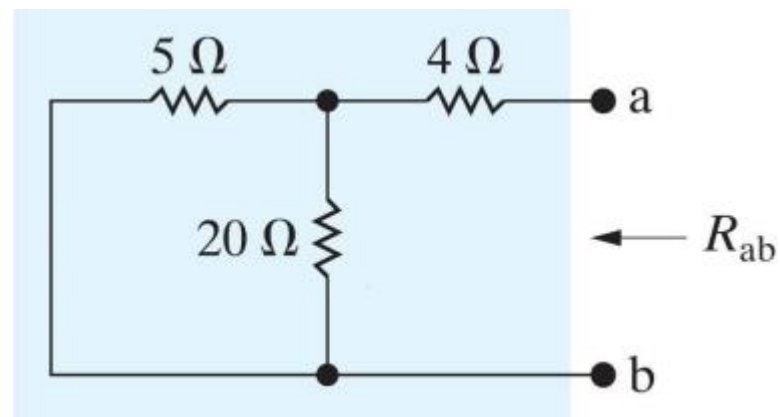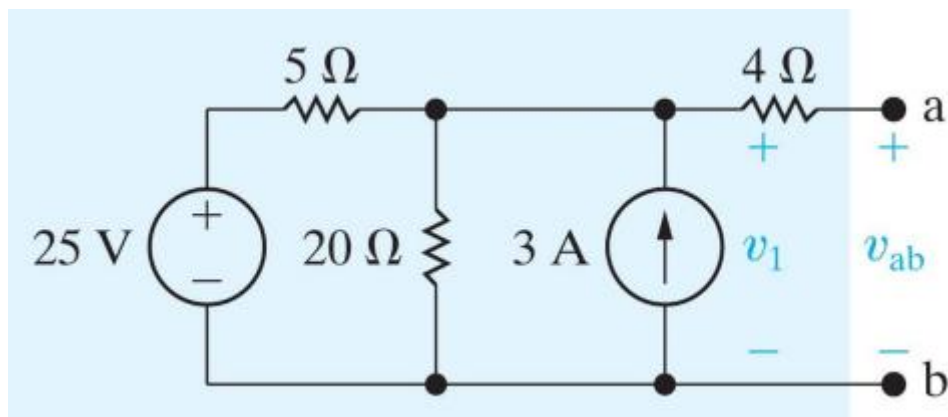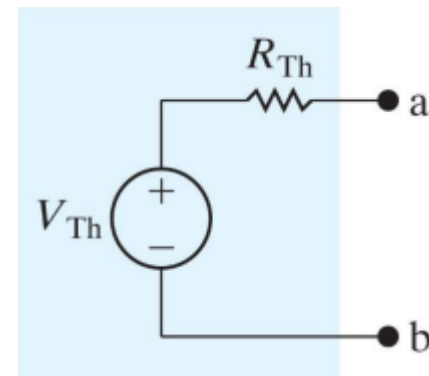
# Thévenin equivalent ckt(4)

- Method 3: finding  $R_{Th}$ 
  - For circuit with **ONLY independent sources**


**Deactivate all sources**  
Voltage source  $\rightarrow$  short  
Current source  $\rightarrow$  open


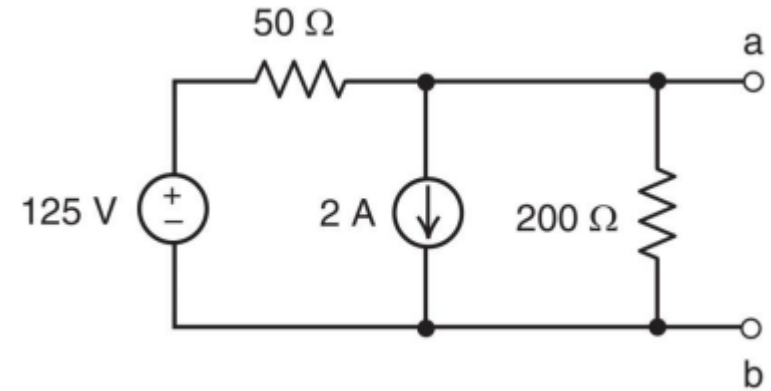
# Thévenin equivalent ckt(5)

---

- Find the Thévenin equivalent circuit
  - Method 1





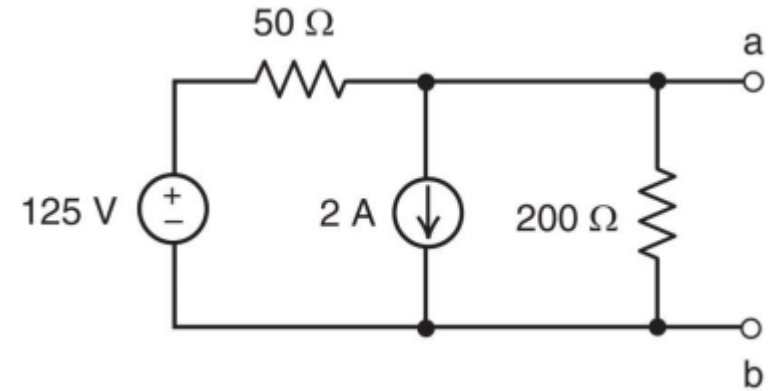
# Thévenin equivalent ckt(6)




---

- Find the Thévenin equivalent circuit
  - Method 2





# Thévenin equivalent ckt(7)

- Find the Thévenin equivalent circuit

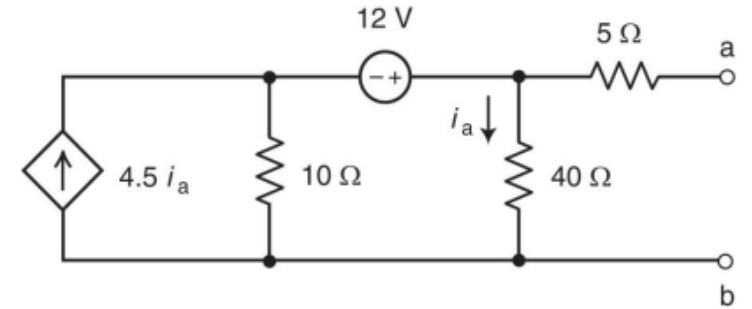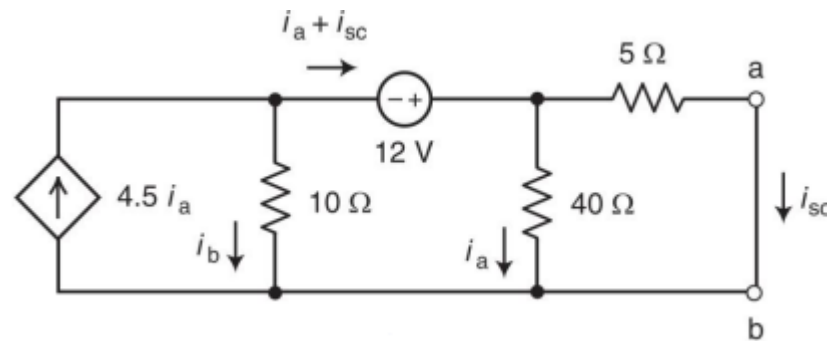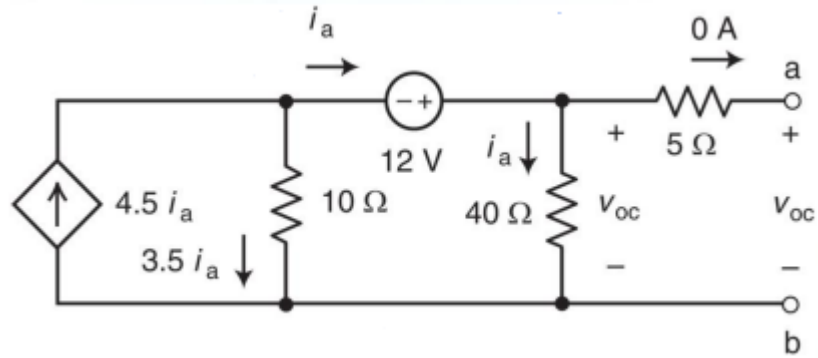
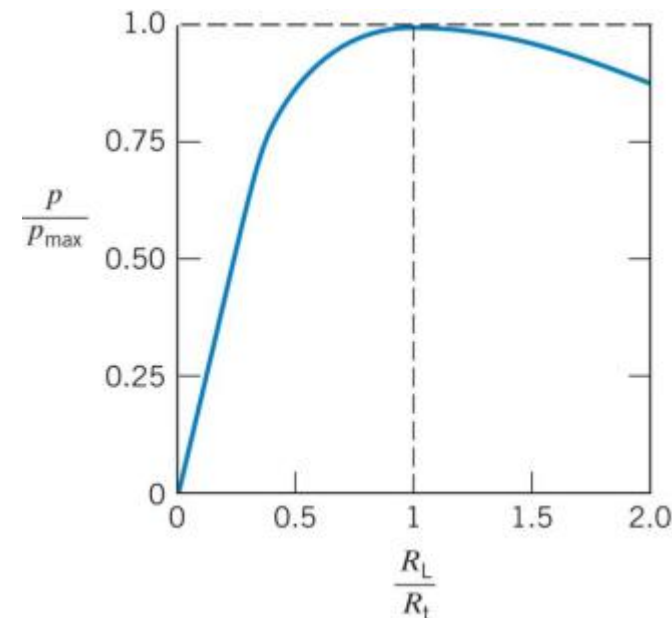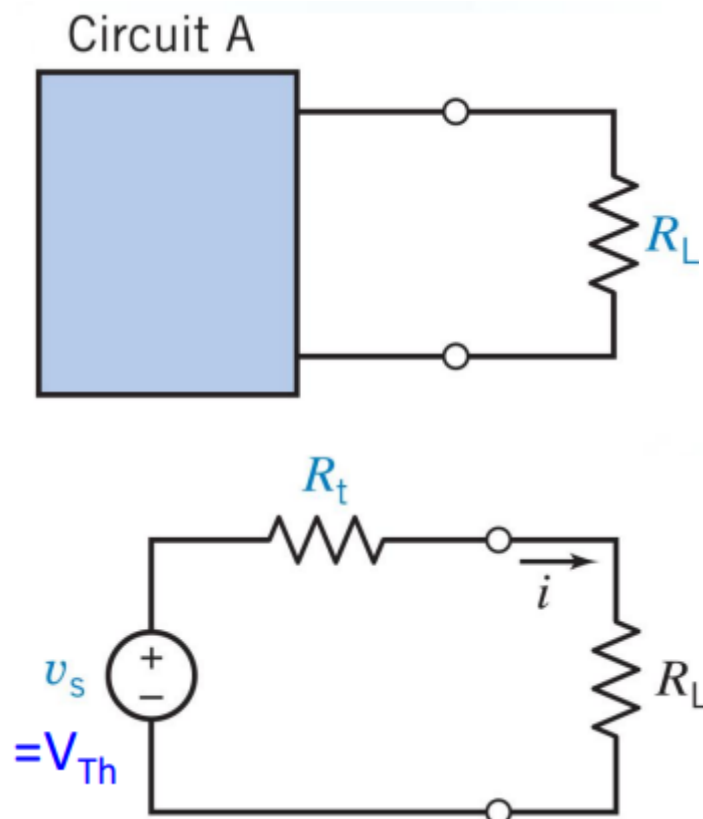
# Maximum power transfer

- Maximum power transfer occurs when  $R_L = R_t$



$$P_{\max} = \frac{V_{Th}^2 R_L}{(2R_L)^2}$$
$$= \frac{V_{Th}^2}{4R_t}$$

# Maximum power transfer

- Find  $R_L$  that will result in maximum power delivery
  - Also determine  $p_{\max}$  delivered to the load resistor

