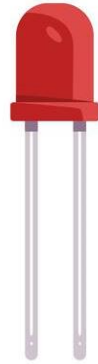


# TOPIC #2 RLC

---



RESISTOR




LED



INDUCTOR



BATTERY

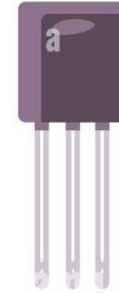


TRANSISTOR



CAPACITOR



DIODE

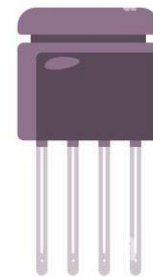


RELAY



IC

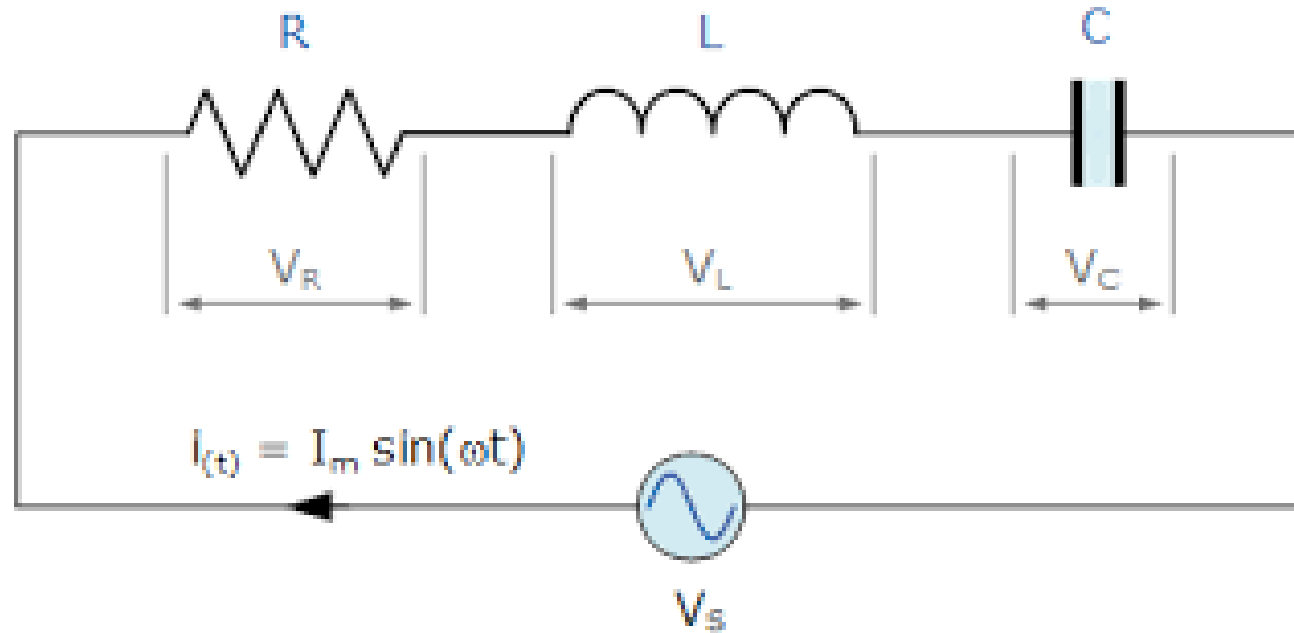
# Introduction of RLC

- R : Resistor 電阻
- L : Inductor 電感 <- Lenz's law
- C : Capacitor 電容


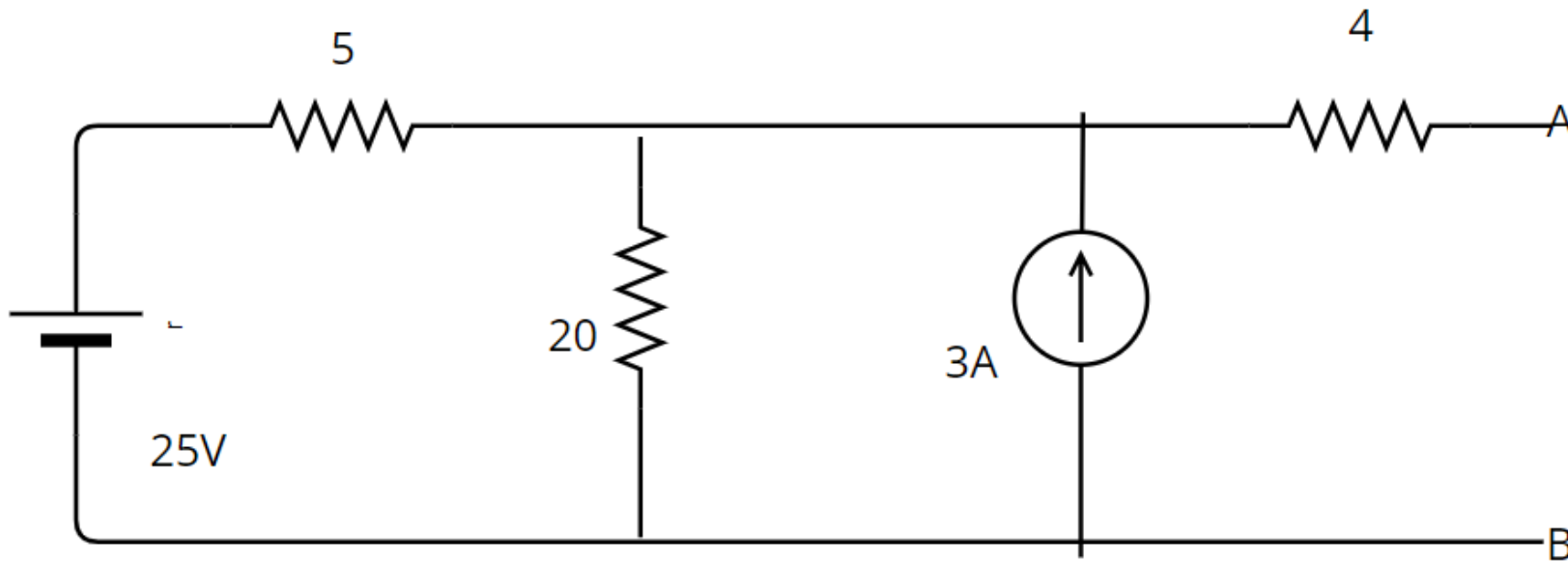
# Voltage/ Current

- Def :  $V = dw/dq$ ,  $I = dq/dt$
- Note: When discussing the voltage, we often simplify the difference of voltage to voltage. Thus, keep in mind that the concept of “difference” is very important to circuit analysis



# Resistor

---

- Always be a **passive device (consuming energy)**
- Commonly used in all circuit
- Covert the electrical energy to thermal energy
- We usually consider the load as a resistor

$$I = \frac{V}{R}$$

$I$  = Current in Amperes (A)  
 $V$  = Voltage in Volts (V)  
 $R$  = Resistance in Ohms ( $\Omega$ )

$$R = \frac{\rho L}{A}$$

$\rho$  = resistivity  
 $L$  = length  
 $A$  = cross sectional area

# Inductor

---

- Not so important
- Store magnetic energy
- Note: the magnetic theorem is more complex than electrical theorem  
It includes a lot concept of PDE(Partial Derivative Equation)
- Refer to these class
  - General physics
  - Electromagnetic
  - Electrical circuit

# Capacitor(1/3)

---

- Def:  $C = Q/V$ 
  - C: Capacitance (unit: F), Q: Charge (unit: coulomb) V: Voltage (unit : volt)
  - 白話:
- In parallel plate  $C = \epsilon \frac{A}{d}$
- Stores electrical energy


# Capacitor(2/3)

---


- In CKT:  $I = C \frac{dV}{dt}$
- This formula gives us some property of capacitor
  1. Since C is proportional to  $dV/dt$ , the voltage difference of capacitors may not vary too much >> Voltage stability
  2. The physical meaning of the above point is that it may take some time to charge/ discharge the capacitor.
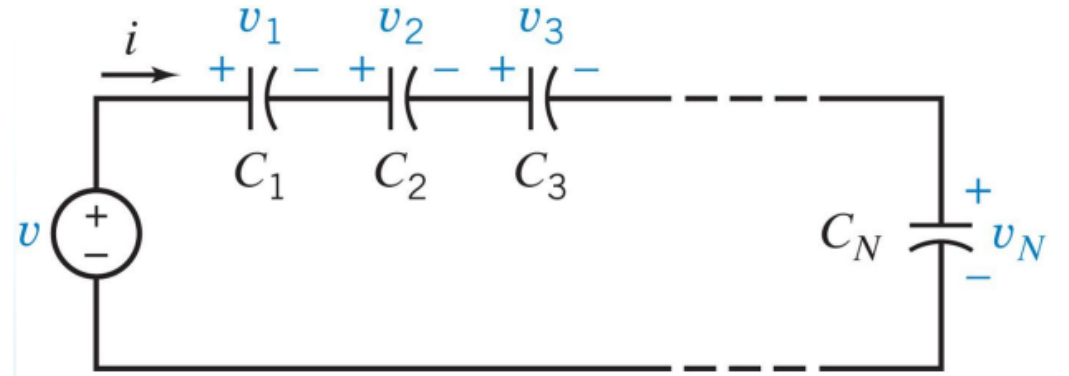
# Capacitor(3/3)

- Capacitor in series:  $\frac{1}{C_{total}} = \sum_i \frac{1}{C_i}$



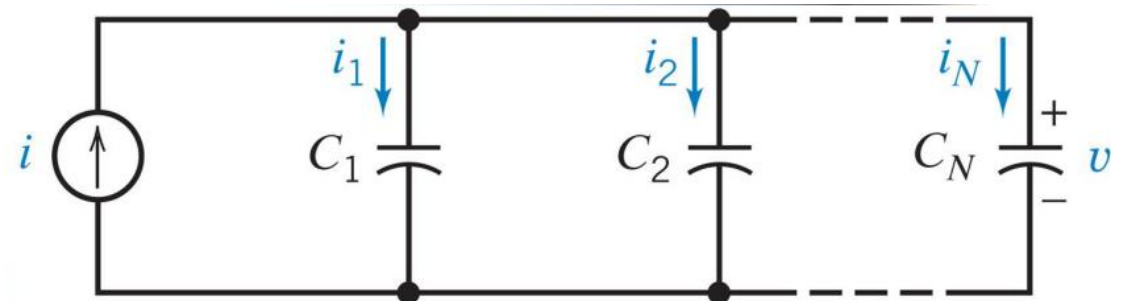
- Capacitor in parallel:  $C_{total} = \sum_i C_i$





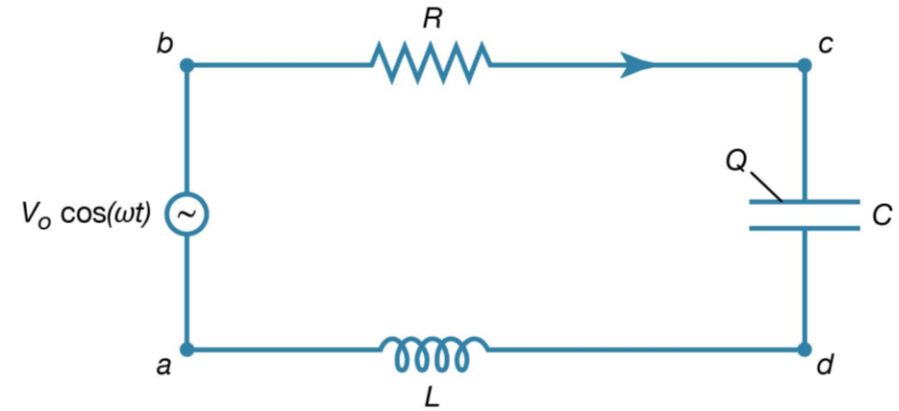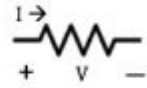
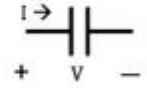

# DC and AC circuit

- DC circuit
  - Simpler
  - The input of the signal may not change with time
  - No frequency response
- AC circuit
  - More complex
  - The input of the signal may be the function of time. Ex:  $\sin(t)$ , square wave, etc.
  - Frequency response
- Frequency response
  - It means that the output of the circuit may vary with different frequency input
  - It may contain complex number computation



# Impedance(1/7)

- The above discussion put more emphasis on the DC circuit
- However, in AC circuit, there are something difference from DC circuit
- We know that the resistance in DC circuit means the ability to block the current flowing through the resistor at given voltage.
- You can believe that the impedance is the resistance of the electric component in AC circuit
- Hard but very important


Circuit Element	Symbol	Current-Voltage Relationship in Time	Impedance
Resistor		$V = IR$	$R$
Capacitor		$I = C \frac{dV}{dt}$	$\frac{1}{j\omega C}$
Inductor		$V = L \frac{dI}{dt}$	$j\omega L$

# Impedance(2/7)

- Euler formula :

$$e^{j\theta} = \cos(\theta) + j \sin(\theta) \text{ where } j = \sqrt{-1}$$

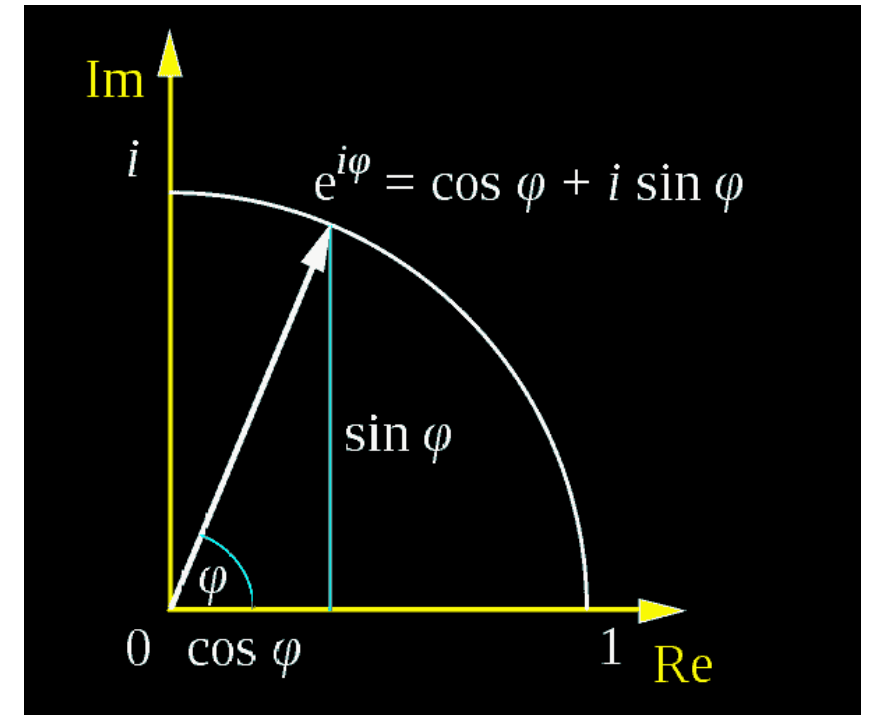- It can be proved by Taylor series expansion
- $e^{j\theta}$  is a unit circle(單位圓) in complex plane
- $\theta$  is the angle between the vector and the real value axis
- $d(e^x)/dx = e^x$



# Impedance(3/7)

---

- Proof of Euler formula

# Impedance(4/7)

---

- Proof of  $d(e^x)/dx = e^x$
- Proof of  $d \sin(x)/dx = \cos(x)$

# Impedance(5/7)

---

- Frequency response of capacitor

# Impedance(6/7)


---

- Frequency response of inductor
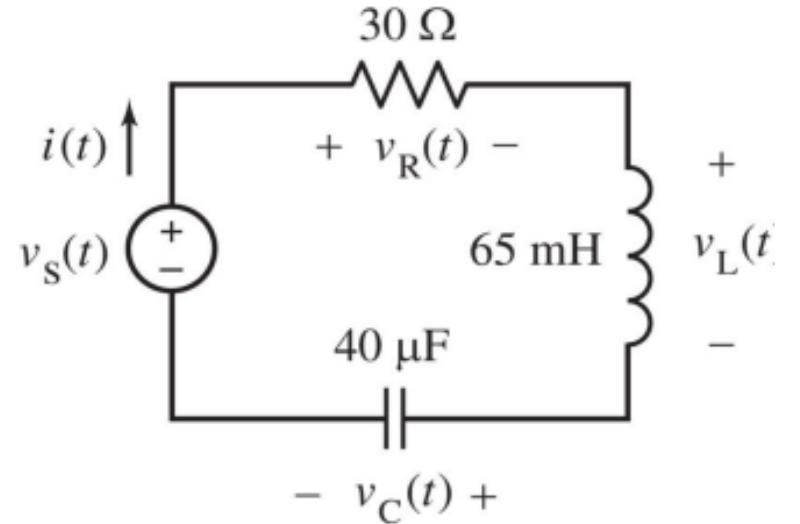
# Impedance(7/7)

- Determine
  - (a) the impedances of the capacitor, inductor, and resistance and
  - (b) the current  $i(t)$


$$v_S(t) = 12 \cos(1000t + 15^\circ) \text{ V}$$




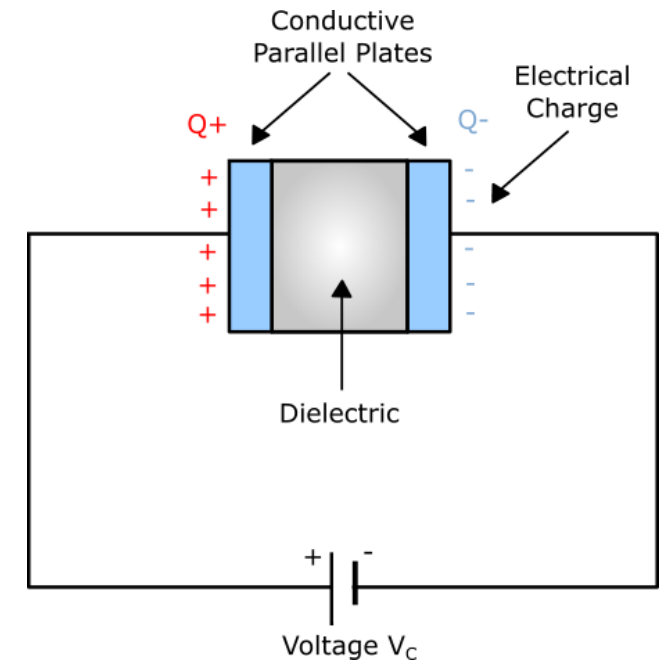
# Take away message

- With DC signal: C can be seen as “open”
  - Because for steady state, C is well charged. The charge on the capacitor will block the current ( $Z = \infty$ )
- With AC signal: C can be seen as “short”
  - In AC circuit, the capacitor may keep charging and discharging, there is always current flowing through the capacitor ( $Z = 0$ )
- With DC signal: L can be seen as “short”
  - Inductor itself is a curl, so it may be seen as a conductive line for steady state. ( $Z = 0$ )
- With AC signal: L can be seen as “open”
  - Because for AC Signal, the curl structure may increase the ability to block the current ( $Z = \infty$ )



Application:  
Filter (濾波器)