 


TOPIC #1 Logic Design

Logic Gate Symbols



OR



NOR



AND



NAND



XOR



XNOR



Buffer




NOT


Introduction

- Analog vs Digital
Continuous and discrete
- The analog world or the digital world?

Analog Signal

 


VS

 

Digital Signal

Why we need digital system

 - Digital signal is more **robust** than the analog one
- Digital signal is easy to be used (store and operate)



Computer Arithmetic

- Skip

Boolean Algebra (1/4)

- Logic algebra
A kind of algebra about 0 and 1
- But! What is algebra?
 $AB =? BA$; $x+y=z$ and $x+w=z \Rightarrow? y=w$
- Any operation don't follow the postulate(公設) / axiom (公理) must be proved
- Any theorem is derived from another theorem or postulate/axiom.

Boolean Algebra (2/4)

1. Closure with respect to “+” and “•”

2. An identity element with respect to “+” and “•”.

$$x + 0 = 0 + x = x \text{ and } x \bullet 1 = 1 \bullet x = x$$

3. Commutative with respect to “+” and “•”

$$x + y = y + x \text{ and } x \bullet y = y \bullet x$$

4. Distributive over “+” and “•”.

$$x \bullet (y + z) = (x \bullet y) + (x \bullet z) \text{ and } x + (y \bullet z) = (x + y) \bullet (x + z)$$

5. For $x \in B$, there exists $x' \in B$ (complement of x) such that

$$x + x' = 1 \text{ and } x \bullet x' = 0.$$

6. There exist at least two elements $x, y \in B$, such that $x \neq y$.

Boolean Algebra (3/4)

Pos. 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Pos. 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Thm. 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Thm. 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Thm. 3, involution	(a)	$(x')' = x$	(b)	
Pos. 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Thm. 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Pos. 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Thm. 5, DeMorgan	(a)	$(x + y)' = x' \cdot y'$	(b)	$(xy)' = x' + y'$
Thm. 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

Boolean Algebra (4/4)

- Thm. 1(a): $x + x = x$

- Thm. 1(b): $x \bullet x = x$

Boolean Algebra (4/)

- Thm. 2: $x + 1 = 1$
- Thm. 6: $x + xy = x$

DeMorgan's Law(1/3)

- $(x + y)' = x' \cdot y'$ (General)

To prove the two set are equivalent, we use **Elementwise method**.

DeMorgan's Law(2/3)

- $(x + y)' = x' \cdot y'$

DeMorgan's Law(3/3)

- $(x \bullet y)' = x' + y'$
 - Homework

Simplification of Boolean Algebra

1. Mathematical way
 - Not intuitive, complicate
2. Truth table
 - Easy, but may not be the simplest circuit.
 - Used with K-Map
3. Karnaugh map
 - Easy, often used in Logic design course but the number of the parameters may not exceed 6.
4. Other ways

Truth Table(1/3)

x	y	$x + y$
0	0	0
0	1	0
1	0	0
1	1	1

AND Logic

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

OR Logic

x	x'
0	1
1	0

NOT Logic

Truth Table(2/3)

- Example

- $F_1 = x + y'z$

- $F_2 = x'y'z + x'yz + xy'z' + xy'z$
 $= x'y'z + x'yz + xy'$

x	y	z	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

Truth Table(3/3)


- Simplify $F = x'y'z + x'yz + xy' = x'z(y' + y) + xy' = x'z + xy'$

Karnaugh map

- There are some details to discuss
- Skip but refer to [清大開放式課程 數位邏輯設計](#)

Logic Gate (1/2)

2 - input AND gate

 


A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

2 - input OR gate



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

 

Input	Output
0	1
1	0

Logic Gate (2/2)

2 - input NAND gate



A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

2 - input NOR gate




A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR gate



A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Exercise 1

 

Exercise 2-1(algebra)

- $F = ((AB)' + A')B + A$

Exercise 2-2(K-Map)

- $F = ((AB)' + A')B + A$

Exercise 3-1 (algebra)


- $F = (A+BC)(A+B)'$

Exercise 3-2 (K-Map)

- $F = (A+BC)(A+B)'$


Combination/ Sequential Logic

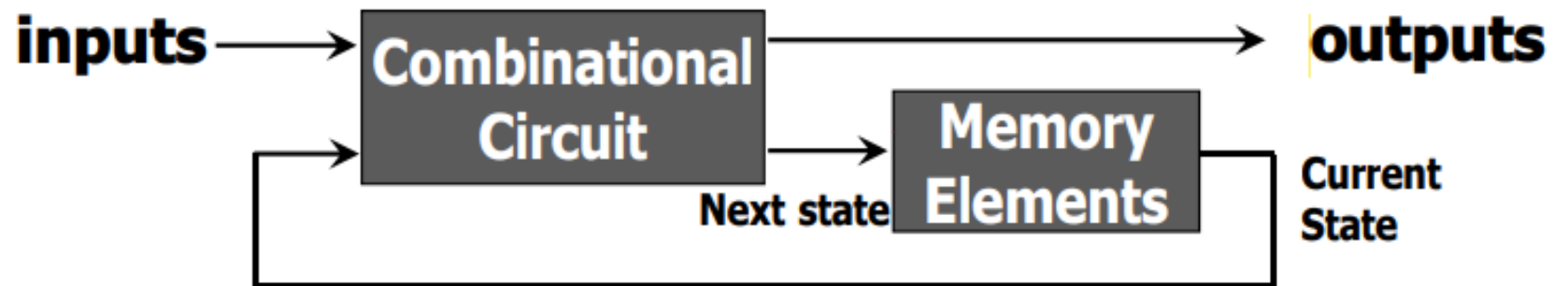- Combinational circuits contain no memory elements, and the outputs depend on the current inputs.
- Designing the sequential logic, you need to consider “clock” well. The main element in sequential logic is memory devices. And we will only introduce Flip-Flop.



Latch(1/3)

 - Latch is a logic device that it can help us be able to control signal well.
- Latch is an asynchronous sequential circuit. (state changes whenever inputs change).



(a) Logic diagram

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	(forbidden)

(b) Function table


Latch(2/3)

 - Exercise: Draw the output of an SR latch for the input waveforms shown below.



Latch(3/3)

- D Latch
 - D latch can eliminate the undesirable condition of the indeterminate state in the SR latch
 - $D \gg Q$ when $En = 1$; no change when $En = 0$
 - A transparent latch when $En = 1$, then $D \gg Q$



En = 0, No change
En = 1, Q = D

Trigger

- A trigger


- The change of the output state of a latch or flip-flop is enabled by a change of the control input (Enable). This momentary change is called trigger.

- Level triggered



- The state transition starts as soon as clock(Enable) is during logic 1 or logic 0 level.
- The change of input makes the combination logic keep changing with the input latch at logic 1 or logic 0.


- Edge triggered

 


- The state transition starts only at positive or negative edge of the clock signal.
- The edge triggered flip-flops will isolate the input changes (current state) and output driving logic (previous state).

Flip-Flop(1/4)

- D Flip-Flop
 - Edge-Triggered

 


(a) Positive-edge

 



(a) Negative-edge

Flip-Flop(2/4)

 
- Exercise: Please plot the graph of D-FF and D-latch according to the following plot.



Flip-Flop(3/4)

  

Flip-Flop(4/4)

 

Homework

- 1
- 2(a)(c)
- 3
- 4
- 5